

**C.B.C.S.S. - B.Sc. DEGREE EXAMINATION, APRIL 2011****Fourth Semester****Core Course—ELECTRONICS**

(Common for B.Sc. Physics Model I, B.Sc. Physics Model II, B.Sc. Physics—EEM  
B.Sc. Physics—Instrumentation)

Time : Three Hours

Maximum Weight : 25

- Notes :**
1. Time allotted for the examination is 3 hours.
  2. Answer all questions in Part A, any five from Part B, any four from Part C and any two from Part D.
  3. Candidates can use scientific, non-programmable calculators / Mathematical tables.

**Part A**

Answer all questions.

This part contains 4 bunches of 4 objective / one answer type questions.  
For each bunch, Grade A will be awarded if all the 4 answers are correct,  
B for 3, C for 2, D for 1 and E for 0.  
Weight 1 each for every bunch.

**BUNCH 1**

Choose the most appropriate alternative :

1. When a PN junction is forward biased :
  - (a) there is no movement of carriers.
  - (b) majority carriers from each region are injected into the other region.
  - (c) only holes from P region are injected into N region.
  - (d) only electrons from N region are injected into P region.
2. The potential barrier existing across a PN junction :
  - (a) prevents flow of minority carriers.
  - (b) prevents neutralization of acceptor and donor atoms.
  - (c) prevents total recombination of holes and electrons.
  - (d) facilitates recombination of holes and electrons.
3. Maximum rectifying efficiency of half wave rectifier is :

(a) 0.812.	(b) 1.21.
(c) 50.	(d) 0.406.

Turn over

4. Zener breakdown occurs :

- (a) mostly in germanium diodes.
- (b) in lightly doped junctions.
- (c) due to thermally generated minority carriers.
- (d) due to rupture of covalent bonds.

BUNCH 2

5. In a properly biased NPN transistor, most of the electrons from the emitter :

- (a) recombine with holes in base.
- (b) recombine with holes in emitter.
- (c) are stopped by the junction barrier.
- (d) pass to the collector through the base.

6. In an amplifier, the coupling capacitors are employed for :

- (a) limiting the bandwidth.
- (b) matching the impedances.
- (c) controlling the output.
- (d) preventing of d.c. mixing with input or output.

7. Transformer coupling is used in class A amplifier so as to make it :

- (a) less bulky.
- (b) less costly.
- (c) distortion free.
- (d) more efficient.

8. Ideal op-amp has input impedance of :

- (a)  $1\text{ m}\Omega$ .
- (b)  $1\ \Omega$ .
- (c) zero.
- (d) infinity.

BUNCH 3

9. For generating a 1 kHz signal, the most suitable circuit is :

- (a) Untuned collector oscillator.
- (b) Hartley oscillator.
- (c) Colpitts oscillator.
- (d) Wien-Bridge oscillator.

10. In an RC phase-shift oscillator, the minimum number of RC networks to be connected in cascade will be :

- (a) 1.
- (b) 2.
- (c) 3.
- (d) 4.

11. The modulation index of an AM wave is changed from 0 to 1. The transmitted power is :

- (a) unchanged.
- (b) halved.
- (c) doubled.
- (d) increased by 50%



12. AM is used for radio broadcasting because :
- (a) it is more immune to noise than other modulation systems.
  - (b) compared with other systems it required less transmitting power.
  - (c) its use avoids receiver complexity.
  - (d) no other modulation system can provide the necessary bandwidth for high fidelity.

## BUNCH 4

13. An FM signal with a modulation index  $m_f$  is passed through a frequency tripler. The wave in the outlet of the tripler will have a modulation index of :
- (a)  $mf/3$ .
  - (b)  $m_f$
  - (c)  $3m_f$
  - (d)  $9m_f$
14. When the modulating frequency is doubled, the modulation index is halved, and the modulating voltage remains constant. The modulation system is :
- (a) amplitude modulation.
  - (b) frequency modulation.
  - (c) phase modulation.
  - (d) any one of the three.
15. A clipper circuit always :
- (a) needs a d.c. source.
  - (b) clips some part of the input signal.
  - (c) clips upper portion of the input signal.
  - (d) clips both half cycles of the input signal.
16. The primary function of a clamper circuit is to :
- (a) suppress the variations in the signal voltage.
  - (b) raise the positive half cycle of the signal.
  - (c) lower the negative half cycle of the signal.
  - (d) introduce a d.c. level into an a.c. signal.

(4 × 1 = 4 weight)

**Part B (Short Answer Type Questions)***Answer any five questions.**Weight 1 each.*

17. Sketch the forward and reverse characteristics of a silicon diode.
18. What is PIV ? Write its value for HWR, bridge and centre tapped rectifier ?
19. Which rectifier filter gives ripple factor independent of the load ? Give reasons.

Turn over

20. What are the conditions to be followed when a voltage multiplier circuit is used ?
21. Compare the input resistances of CB and CE configurations, giving typical values.
22. What is cross-over distortion ? Which circuit shows the same and how it can be eliminated ?
23. What happens to the input and output resistances of an amplifier when a negative voltage-series feedback is used ?
24. Draw a voltage follower circuit using op-amp and express its  $R_i$  and  $R_o$ .

(5 × 1 = 5 weight)

### Part C (Short Essays/Problems)

*Answer any four questions.*

*Weight 2 each.*

25. Draw the Zener shunt voltage regulator. Design it for an output voltage 5 V, max : load current 20 mA.
26. Draw the circuit of a voltage tripler and explain its working.
27. Define  $\alpha$  and  $\beta$  and derive the relationship between them. Calculate  $I_c$  of a transistor whose  $I_B = 12 \mu\text{A}$  and  $\alpha = 0.993$ .
28. What is virtual ground in an op-amp ? What are the conditions to maintain the same ?
29. Draw the circuit diagram of a Colpitts oscillator. Calculate its frequency when  $C_1 = 10 \text{ pF}$  and  $C_2 = 22 \text{ pF}$  and  $L = 100 \mu\text{H}$ .
30. A broad cast AM transmitter radiates 100 W of carrier power. What will be the radiated power at 70% modulation ?

(4 × 2 = 8 weight)

### Part D (Essays Type Questions)

*Answer any two questions.*

*Each question carries a weight of 4.*

31. Draw the complete circuit diagram (as a single connected unit) of a power supply. It uses a bridge rectifier, a  $\pi$  filter and a Zener shunt regulator. Briefly explain the working of each component in it.
32. Draw the experimental set up to obtain the input and output VI characteristics of a CB configuration. With the help of the neat sketch, describe the shapes of the characteristics.
33. With a neat circuit diagram, explain how Barkhausen criteria are satisfied in an RC phase-shift oscillator ?

(2 × 4 = 8 weight)