

**B.Sc. DEGREE (C.B.C.S.S) EXAMINATION, MARCH/APRIL 2012****Fourth Semester****Core Course—ELECTRONICS**

(Common for B.Sc. Physics Model I, B.Sc. Physics Model II, B.Sc. Physics—EEM and  
B.Sc. Physics—Instrumentation)

Time : Three Hours

Maximum Weight : 25

**Notes :** 1. Time allotted for the examination is 3 hours.

2. Answer all questions in Part A, any five from Part B, any four from Part C and any two from Part D.

3. Candidates can use scientific, non-programmable calculators/ Mathematical tables.

**Part A**

Answer all questions.

This part contains 4 bunches of 4 objective/one answer type questions.

For each bunch, Grade A will be awarded if all the 4 answers are correct,

B for 3, C for 2, D for 1 and E for 0.

Weight 1 each for every bunch.

**BUNCH 1**

Choose the most appropriate alternative :

1. The depletion region or space charge region or transition region in a semiconductor PN junction diode has :
  - (a) Electrons and holes.
  - (b) Positive ions and negative ions.
  - (c) Positive ions and electrons.
  - (d) No ions, electrons or holes.
2. The minority carrier concentration in a diode is largely a function of :
  - (a) Reverse biasing voltage.
  - (b) Forward biasing voltage.
  - (c) Temperature.
  - (d) The amount of doping.
3. In a Zener diode, large reverse current is due to :
  - (a) Collision.
  - (b) Presence of impurities.
  - (c) Rupture of bonds.
  - (d) Lower resistance in reverse biased region.
4. If the output voltage of a bridge rectifier is 100 V, the PIV of the diode will be :
  - (a)  $100\sqrt{2}$  V.
  - (b)  $100\pi$  V.
  - (c)  $50\pi$  V.
  - (d)  $\frac{200}{\pi}$  V.

**Turn over**

## BUNCH 2

5. The main component responsible for lowering of gain in an RC coupled amplifier in low frequency range is :
- (a) Biasing system.
  - (b) Resistor  $R_E$ .
  - (c) Coupling capacitor  $C_C$ .
  - (d) Transistor itself.
6. In cascading amplifiers the intermediate stage is :
- (a) CB.
  - (b) CE.
  - (c) CC.
  - (d) None of the above.
7. Class AB operation is often used in power amplifiers in order to :
- (a) Get maximum efficiency.
  - (b) Remove even harmonics.
  - (c) Overcome cross-over distortion.
  - (d) Reduce collector dissipation.
8. An ideal op-amp is used to make an inverting amplifier. The two input terminals of the op-amp are at the same potential because :
- (a) The two input terminals are directly shorted internally.
  - (b) The open loop voltage gain of the op-amp is infinity.
  - (c) CMRR is infinity.
  - (d) Both (b) and (c).

## BUNCH 3

9. An ideal amplifier is one which :
- (a) Has infinite voltage gain.
  - (b) Responds only to signal at its input terminals.
  - (c) Has positive feedback.
  - (d) Gives uniform frequency response.
10. Unique features of a CC amplifier circuit is that it :
- (a) Steps up the impedance level.
  - (b) Does not increase signal voltage.
  - (c) Acts as an impedance matching device.
  - (d) All of the above.
11. If properly biased, JFET will act as a :
- (a) Current controlled voltage source.
  - (b) Current controlled current source.
  - (c) Voltage controlled voltage source.
  - (d) Voltage controlled current source.



12. The only drawback of using negative feedback in amplifiers is that it involves :

- (a) Gain stability. (b) Gain sacrifice.
- (c) Frequency dependence. (d) Temperature sensitivity.

BUNCH 4

13. If Barkhausen criterion is not fulfilled by an oscillator circuit, it will :

- (a) Produce high-frequency whistles.
- (b) Produce damped waves continuously.
- (c) Becomes an amplifier.
- (d) Stops oscillating.

14. The primary advantage of a crystal oscillator is that :

- (a) It can oscillate at any frequency.
- (b) It gives a high output voltage.
- (c) Its frequency of oscillation remains almost constant.
- (d) It operates on very low d.c. supply voltage.

15. A linear diode detector utilizes :

- (a) Linear portion of static characteristics of diode.
- (b) Linear portion of dynamic characteristics of diode.
- (c) Square law portion of dynamic characteristics of diode.
- (d) Rectification property of diode.

16. In the FM wave described by equation  $v = 15 \sin (4 \times 10^8 t + 3 \sin 1100 t)$ , the maximum frequency deviation is :

- (a) 175 Hz. (b) 525 Hz.
- (c) 3 Hz. (d) 58.33 Hz.

(4 × 1 = 4)

**Part B (Short Answer Type Questions)**

*Answer any five questions.*

*Weight 1 each.*

- 17. What are the different types of  $p-n$  junction capacitances ? What are their causes ?
- 18. Distinguish between the centre tapped and bridge rectifiers.
- 19. Draw the circuit diagram of a voltage tripler using diodes.
- 20. Define, basically the three operating regions of a bipolar transistor ?
- 21. Draw the  $h$ -parameter equivalent circuit for a cc configuration, giving typical parameter values.

Turn over

22. List the *four* types of negative feedbacks, giving their block schematics.
23. What is virtual ground in an op-amp circuit? What are the conditions to be satisfied to have the virtual ground in an op-amp circuit?
24. Sketch and label the frequency spectrum of an AM wave when a 625 kHz carrier is modulated by audio waves of 50 Hz to 5 kHz signal.

(5 × 1 = 5)

### Part C (Short Essays/Problems)

*Answer any four questions.*

*Weight 2 each.*

25. A  $\Lambda$  -  $\pi$  filter in a full wave rectifier uses  $C_1 = C_2 = 470 \mu\text{F}$  and  $L = 10 \text{ H}$ . The load current is 300 mA at 100 V dc. Calculate the ripple factor.
26. Determine (a) the applied voltage to achieve a forward current of  $0.45 \mu\text{A}$  in a *pn* junction Si diode at  $T = 300 \text{ K}$ , if the reverse saturation current is  $1.0 \text{ nA}$ . (b) If the reverse saturation current in a Ge diode is  $10 \mu\text{A}$ , what current would result if the voltage in part (a) is applied in the forward direction?
27. Calculate the d.c. bias currents and voltages for a voltage divider bias circuit having  $R_1 = 40 \text{ K}$ ,  $R_2 = 10 \text{ K}$ ,  $R_C = 1.5 \text{ K}$ ,  $R_E = 2 \text{ K}$ ,  $V_{CC} = 10 \text{ V}$ ,  $\beta = 100$  and  $V_{BE} = 0.7 \text{ V}$ .
28. A germanium transistor has  $I_{CBO} = 10 \mu\text{A}$ ,  $\alpha = 0.98$  and  $I_C = 1 \text{ mA}$ . Determine the emitter current and  $\beta$  of the transistor.
29. A Hartley oscillator is designed with  $L_1 = 2 \text{ mH}$ ,  $L_2 = 20 \mu\text{H}$  and a variable capacitor. Determine the range of capacitance values, if the frequency of oscillation is varied between 950 and 2050 kHz.
30. A 500 W carrier is simultaneously amplitude modulated by two audio waves with modulation percentage of 50% and 80% respectively. What is the total sideband power radiated?

(4 × 2 = 8)

### Part D (Essay Type Questions)

*Answer any two questions.*

*Weight 4 each.*

31. With a neat circuit diagram, describe how a Zener shunt voltage regulator provides voltage regulation against variations in the input voltage and output current? Design the circuit for an output voltage of 5V, to load upto a maximum of 50 mA.
32. Draw the CE amplifier circuit. Sketch its *h*-parameter equivalent circuit and derive expressions for its voltage and current gains, input and output resistances.
33. With a circuit diagram, explain how sustained sinusoidal oscillations are produced in a RC phase-shift oscillator? Explain the function of each component in the circuit.

(2 × 4 = 8)